



Mini-projet en VHDL

Travail réalisé par :

BOUSELHAM Loubna

MERZOUKI Alae

MOURHLI Med

RABYI Kaoutar

YAHYAOUI Fatima


Département : Génie Electrique

Année universitaire : 2008/2009

Sommaire

Partie 1 : Conception d'un mini-calculateur	3
I. Conception de l'UAL	
- Conception du comparateur 4 bits	4
- Conception de l'UAL	8
II. Conception des registres.....	14
III. Conception des multiplexeurs et démultiplexeurs	
1. Conception des multiplexeurs	
- 2 vers 1.....	17
- 4 vers 1.....	19
2. Conception de démultiplexeur	23
IV. Conception du contrôleur.....	25
V. Conception final du mini-calculateur	27
Partie 2 : Exercices en VHDL	29
I. Modélisation d'un décodeur 7 segments	30
II. Modélisation d'un compteur synchrone	35
III. Modélisation d'une bascule D Flip Flop	38
IV. Modélisation d'une bascule JK	41

Conception d'un mini-calculateur

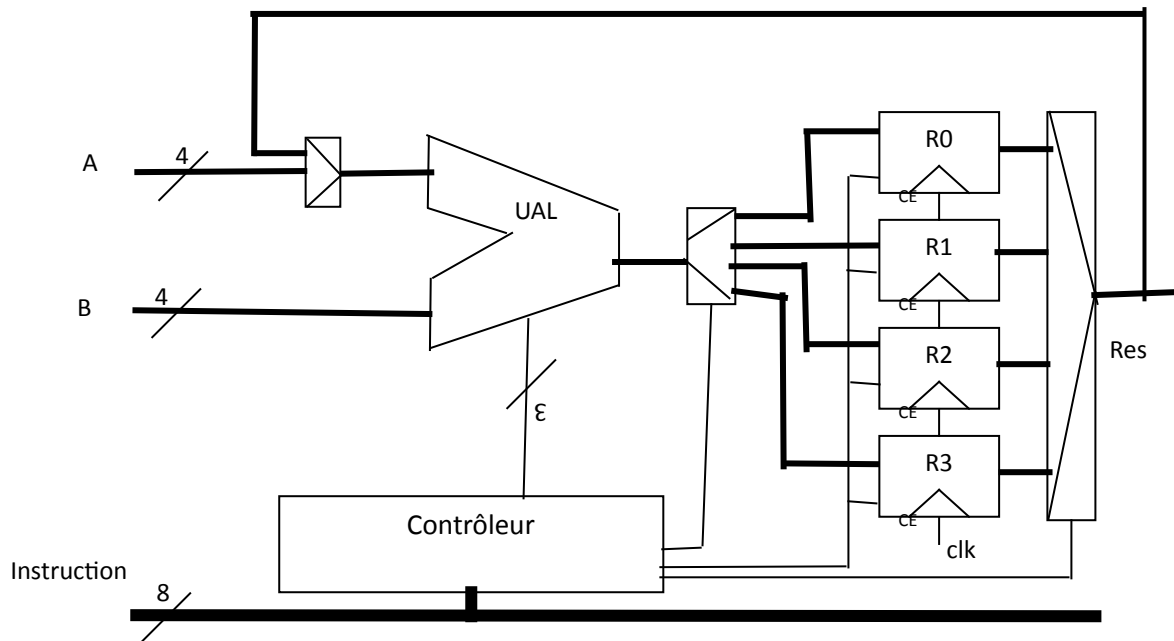

I. Conception de l'Unité arithmétique et logique :

1. Conception du comparateur 4 bits :

a. Table de vérité

Entrées				Sorties		
A3, B3	A2, B2	A1, B1	A0, B0	A_SUP_B	A_INF_B	A_EGAL_B
A3>B3	x	x	x	1	0	0
A3<B3	x	x	x	0	1	0
A3=B3	A2>B2	x	x	1	0	0
A3=B3	A2<B2	x	x	0	1	0
A3=B3	A2=B2	A1>B1	x	1	0	0
A3=B3	A2=B2	A1<B1	x	0	1	0
A3=B3	A2=B2	A1=B1	A0>B0	1	0	0
A3=B3	A2=B2	A1=B1	A0<B0	0	1	0
A3=B3	A2=B2	A1=B1	A0=B0	0	0	1

b. Fichier « compar_4b » :

```

1  LIBRARY ieee;
2  USE ieee.std_logic_1164.all;
3  entity compar_4b is
4  port (A,B :in std_logic_vector(3 downto 0);
5  A_SUP_B,A_INF_B,A_EGAL_B :out std_logic);
6  end compar_4b;
7  architecture arch_compar_4b of compar_4b is
8  begin
9  A_SUP_B <= '1' WHEN A > B ELSE '0';
10 A_INF_B <= '1' WHEN A < B ELSE '0';
11 A_EGAL_B <= '1' WHEN A = B ELSE '0';
12 end arch_compar_4b;

```

On tape les lignes de commande suivantes dans la fenêtre *transcript* :

```

force A 0000 0,1000 40,0000 80,1100 120,0000 160,1110 200,1001 240,1111
280,0100 320,1111 360

```

(On force le signal A à 0000 au temps 0, à 1000 au temps 40, à 0000 au temps 80, à 1100 au temps 120, à 0000 au temps 160, à 1110 au temps 200, à 1001 au temps 240, à 1111 au temps 280, à 0100 au temps 320 et à 1111 au temps 360)


```

force B 0000 0,0000 40,1000 80,1000 120,0100 160,1100 200,1011 240,1110
280,0101 320,1111 360

```

Run 400

 La simulation donne les résultats suivants:



c. Fichier « compar_4b_TB » :

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  entity compar_4b_TB is
4  end compar_4b_TB;
5  architecture TB1 of compar_4b_TB is
6  component compar_4b
7      port (A,B : in std_logic_vector (3 downto 0);
8            A_SUP_B,A_INF_B,A_EGAL_B :out std_logic);
9  end component;
10 signal A, B: std_logic_vector ( 3 downto 0);
11 signal A_SUP_B,A_INF_B,A_EGAL_B : std_logic;
12 begin
13     compar: compar_4b port map (A, B,A_SUP_B,A_INF_B,A_EGAL_B);
14     process
15         variable C:integer :=0;
16         begin
17             --case1:A3>B3
18             A <= "1000";
19             B <= "0100";
20             wait for 10ns;
21             assert (A_SUP_B ='1') report "SUP Error!" Severity error;
22             assert (A_INF_B='0') report "INF Error!" Severity error;
23             assert (A_EGAL_B='0') report "EGAL Error!" Severity error;
24             if(A_SUP_B/='1' or A_INF_B/='0' or A_EGAL_B/='0') then
25                 C:=C+1;
26             end if;
27             -- case2: A3<B3
28             A <= "0000";
29             B <= "1100";
30             wait for 10ns;
31             assert (A_SUP_B='0') report "SUP Error!" Severity error;
32             assert (A_INF_B='1') report "INF Error!" Severity error;
33
34             assert (A_EGAL_B='0') report "EGAL Error!" Severity error;
35             if(A_SUP_B/='0' or A_INF_B/='1' or A_EGAL_B/='0') then
36                 C:=C+1;
37             end if;
38
39             -- case3: A3=B3 A2>B2
40             A <= "0100";
41             B <= "0010";
42             wait for 10ns;
43             assert (A_SUP_B='1') report "SUP Error!" Severity error;
44             assert (A_INF_B='0') report "INF Error!" Severity error;
45             assert (A_EGAL_B='0') report "EGAL Error!" Severity error;
46             if(A_SUP_B/='1' or A_INF_B/='0' or A_EGAL_B/='0') then

```


```

47     -- case4:A3=B3 A2<B2
48     A <= "0001";
49     B <= "0110";
50     wait for 10ns;
51     assert (A_SUP_B='0') report "SUP Error!" Severity error;
52     assert (A_INF_B='1') report "INF Error!" Severity error;
53     assert (A_EGAL_B='0') report "EGAL Error!" Severity error;
54     if(A_SUP_B/'0' or A_INF_B/'1' or A_EGAL_B/'0') then
55         C:=C+1;
56     end if;
57     -- case5:A3=B3 A2=B2 A1>B1
58     A <= "0111";
59     B <= "0100";
60     wait for 10ns;
61     assert (A_SUP_B='1') report "SUP Error!" Severity error;
62     assert (A_INF_B='0') report "INF Error!" Severity error;
63     assert (A_EGAL_B='0') report "EGAL Error!" Severity error;
64     if(A_SUP_B/'1' or A_INF_B/'0' or A_EGAL_B/'0') then
65         C:=C+1;
66     end if;
67     -- case6:A3=B3 A2=B2 A1<B1
68     A <= "0101";
69     B <= "0110";
70     wait for 10ns;
71     assert (A_SUP_B='0') report "SUP Error!" Severity error;
72     assert (A_INF_B='1') report "INF Error!" Severity error;
73     assert (A_EGAL_B='0') report "EGAL Error!" Severity error;
74     if(A_SUP_B/'0' or A_INF_B/'1' or A_EGAL_B/'0') then
75         C:=C+1;
76     end if;


77     -- case7:A3=B3 A2=B2 A1=B1 A0>B0
78     A <= "0101";
79     B <= "0100";
80     wait for 10ns;
81     assert (A_SUP_B='1') report "SUP Error!" Severity error;
82     assert (A_INF_B='0') report "INF Error!" Severity error;
83     assert (A_EGAL_B='0') report "EGAL Error!" Severity error;
84     if(A_SUP_B/'1' or A_INF_B/'0' or A_EGAL_B/'0') then
85         C:=C+1;
86     end if;
87     -- case8:A3=B3 A2=B2 A1=B1 A0<B0
88     A <= "0100";
89     B <= "0101";
90     wait for 10ns;
91     assert (A_SUP_B='0') report "SUP Error!" Severity error;
92     assert (A_INF_B='1') report "INF Error!" Severity error;
93     assert (A_EGAL_B='0') report "EGAL Error!" Severity error;
94     if(A_SUP_B/'0' or A_INF_B/'1' or A_EGAL_B/'0') then
95         C:=C+1;
96     end if;
97     -- case9:A3=B3 A2=B2 A1=B1 A0=B0
98     A <= "0101";
99     B <= "0101";
100    wait for 10ns;
101    assert (A_SUP_B='0') report "SUP Error!" Severity error;
102    assert (A_INF_B='0') report "INF Error!" Severity error;
103    assert (A_EGAL_B='1') report "EGAL Error!" Severity error;
104    if(A_SUP_B/'0' or A_INF_B/'0' or A_EGAL_B/'1') then
105        C:=C+1;
106    end if;

```

 La simulation donne les résultats suivants:



2. Conception de l'UAL :

 

a. Fichier « Operations.vhd » :

Le champ CodeOp sert à indiquer la nature de l'opération à réaliser :

CodeOP	Opération à réaliser
000	Resultat <= A ET B
001	Resultat <= A NON ET B
010	Resultat <= A OU B
011	Resultat <= A NON OU B
100	Resultat <= A XOR B
101	Resultat <= NOT A
110	Resultat <= A + B
111	Resultat <= A - B

b. Fichier « Indications.vhd » :

- S_OVFL : sortie permettant d'indiquer si l'opération effectue un débordement.
- S_ZERO : sortie permettant d'indiquer si le résultat est nul.

```

1  LIBRARY ieee;
2  USE ieee.std_logic_1164.all;
3  USE ieee.std_logic_unsigned.all;
4
5  entity operations is
6  port ( A,B: in std_logic_vector(3 downto 0);
7        Code: in std_logic_vector(2 downto 0);
8        RES:out std_logic_vector(3 downto 0));
9  end operations;
10 Architecture arch_operations of operations is
11     begin
12         Op:process (Code)
13             begin
14                 case Code is
15                     when "000" => RES <= A and B;
16                     when "001" => RES <= A nand B;
17                     when "010" => RES <= A or B;
18                     when "011" => RES <= A nor B;
19                     when "100" => RES <= A xor B;
20                     when "101" => RES <= not A;
21                     when "110" => RES <= A + B;
22                     when others => RES <= A - B;
23                 end case;
24             end process Op;
25     end arch_operations;

```


- S_NEG : sortie permettant d'indiquer sur le résultat est négatif.

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_unsigned.all;

entity out_indications is
port (RES:in std_logic_vector(3 downto 0);
      OVFL,NEG,ZERO:out std_logic);
end out_indications;
architecture arch_out_indications of out_indications is
begin
    indic:process(RES)
    begin
        if (RES) > "1111" then OVFL <= '1';
        else OVFL <= '0';
        end if;
        if (RES) < "0000" then NEG <= '1';
        else NEG <= '0';
        end if;
        if (RES) = "0000" then ZERO <= '1';
        else ZERO <= '0';
        end if;
    end process indic;
end arch_out_indications;
```

c. Fichier « Unite.vhd » : description complète de l'UAL :


```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_unsigned.all;
entity Unite is
port ( entree_A,entree_B: in std_logic_vector(3 downto 0);
      CodeOP:in std_logic_vector(2 downto 0);
      resultat:out std_logic_vector(3 downto 0);
      S_A_SUP_B,S_A_INF_B,S_A_EGAL_B,S_NEG,S_ZERO,S_OVFL:out std_logic);
end Unite;
architecture arch_Unite of Unite is
  signal Y:std_logic_vector(3 downto 0);
component compar_4b
port (A,B :in std_logic_vector(3 downto 0);
      A_SUP_B :out std_logic;
      A_INF_B :out std_logic;
      A_EGAL_B :out std_logic);
end component;
component operations
port ( A,B: in std_logic_vector(3 downto 0);
      Code: in std_logic_vector(2 downto 0);
      RES:out std_logic_vector(3 downto 0));
end component;
component out_indications
  port (RES:in std_logic_vector(3 downto 0);
        OVFL,NEG,ZERO:out std_logic);
  end component;
begin
Op:operations port map(entree_A,entree_B,CodeOp,Y);
resultat <= Y;
c:compar_4b port map(entree_A,entree_B,S_A_SUP_B,S_A_INF_B,S_A_EGAL_B);
Indic:out_indications port map (Y,S_OVFL,S_NEG,S_ZERO);
end arch_Unite;
```

On tape les lignes de commande suivantes dans la fenêtre *transcript* :

```
force entree_A 0000 0,1000 40,0000 80,1100 120,0000 160,1110 200,1001 240,1111
280,0100 320,1111 360
force entree_B 0000 0,0000 40,1000 80,1000 120,0100 160,1100 200,1011 240,1110
280,0101 320,1111 360
```

force CodeOp 000 0,001 40,010 80,011 120,100 160,101 200,110 240,111 360
run 400

 La simulation donne les resultats suivants :



d. Fichier « Unite_TB.vhd » : TestBench de l'UAL :

```

library ieee;
use ieee.std_logic_1164.all;

entity Unite_TB is
end Unite_TB;
architecture TB3 of Unite_TB is
component Unite
port (entree_A,entree_B: in std_logic_vector(3 downto 0);
      CodeOP:in std_logic_vector(2 downto 0);
      resultat:out std_logic_vector(3 downto 0);
      S_A_SUP_B,S_A_INF_B,S_A_EGAL_B,S_NEG,S_ZERO,S_OVFL:out std_logic);
end component;
signal entree_A,entree_B:std_logic_vector(3 downto 0);
signal CodeOP:std_logic_vector(2 downto 0);
signal resultat:std_logic_vector(3 downto 0);
signal S_A_SUP_B,S_A_INF_B,S_A_EGAL_B,S_NEG,S_ZERO,S_OVFL:std_logic;
begin
U: Unite port map (entree_A,entree_B,CodeOP,resultat,S_A_SUP_B,S_A_INF_B,S_A_EGAL_B,S_NEG
process
  variable C:integer :=0;
  begin
  --cas1:
  CodeOp <= "000";
  entree_A <= "1000";
  entree_B <= "0100";
  wait for 10ns;
  assert (resultat ="0000")report "ET Error!" Severity error;
  assert (S_A_SUP_B='1') report "SUP Error!" Severity error;
  assert (S_A_INF_B='0') report "INF Error!" Severity error;
  assert (S_A_EGAL_B='0') report "EGAL Error!" Severity error;
  if (resultat /= "1100"or S_A_SUP_B/= '1' or S_A_INF_B/= '0' or S_A_EGAL_B/= '0')then
    C:=C+1;
  end if;

```

```

-- case4:
CodeOp <= "011";
entree_A <= "0001";
entree_B <= "0110";
wait for 10ns;
assert (resultat ="1000")report "NON_OU Error!" Severity error;
assert (S_A_SUP_B='0') report "SUP Error!" Severity error;
assert (S_A_INF_B='1') report "INF Error!" Severity error;
assert (S_A_EGAL_B='0') report "EGAL Error!" Severity error;
if(resultat /="1000" or S_A_SUP_B/'0' or S_A_INF_B/'1' or S_A_EGAL_B/'0') then
C:=C+1;
end if;
-- case5:
CodeOp <= "100";
entree_A <= "0111";
entree_B <= "0100";
wait for 10ns;
assert (resultat ="0011")report " OU_Exclusive Error!" Severity error;
assert (S_A_SUP_B='1') report "SUP Error!" Severity error;
assert (S_A_INF_B='0') report "INF Error!" Severity error;
assert (S_A_EGAL_B='0') report "EGAL Error!" Severity error;
if(resultat /="0011" or S_A_SUP_B/'1' or S_A_INF_B/'0' or S_A_EGAL_B/'0') then
C:=C+1;
end if;
-- case6:
CodeOp <= "101";
entree_A <= "0101";
entree_B <= "0110";
wait for 10ns;
assert (resultat ="1010")report "NOT Error!" Severity error;
assert (S_A_SUP_B='0') report "SUP Error!" Severity error;
assert (S_A_INF_B='1') report "INF Error!" Severity error;
assert (S_A_EGAL_B='0') report "EGAL Error!" Severity error;
if(resultat /="1010" or S_A_SUP_B/'0' or S_A_INF_B/'1' or S_A_EGAL_B/'0') then
C:=C+1;
end if;

-- case7:
CodeOp <= "110";
entree_A <= "0101";
entree_B <= "0100";
wait for 10ns;
assert (resultat ="1001")report "NOT Error!" Severity error;
assert (S_A_SUP_B='1') report "SUP Error!" Severity error;
assert (S_A_INF_B='0') report "INF Error!" Severity error;
assert (S_A_EGAL_B='0') report "EGAL Error!" Severity error;
if(resultat /="1001"or S_A_SUP_B/'1' or S_A_INF_B/'0' or S_A_EGAL_B/'0') then
C:=C+1;
end if;
-- case8:
CodeOp <="111";
entree_A <= "0101";
entree_B <= "0101";
wait for 10ns;
assert (resultat ="0000")report "Soustraction Error!" Severity error;
assert (S_A_SUP_B='0') report "SUP Error!" Severity error;
assert (S_A_INF_B='0') report "INF Error!" Severity error;
assert (S_A_EGAL_B='1') report "EGAL Error!" Severity error;
if(resultat /="0000" or S_A_SUP_B/'0' or S_A_INF_B/'0' or S_A_EGAL_B/'1') then
C:=C+1;
end if;


```

```

-- summary of testbench
if (C=0) then
  assert false
  report "Testbench of Unite completed successfully!"
  severity note;
else
  assert true
  report " Something wrong,try again"
  severity error;
end if;
wait;
end process;
end TB3;


```

 La simulation donne les résultats suivants :



 II. Conception des registres :

(Registre de mémorisation : Il s'agit en fait d'un ensemble de bascules D flip-flop formant un mot binaire de 4 bits)




```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

entity REGISTRE is
port (clock_enable, CLR, CE :in std_logic;
      D :in std_logic_vector(3 downto 0);
      Q :out std_logic_vector(3 downto 0));
end REGISTRE;
architecture ARCH_REGISTRE of REGISTRE is
signal X :std_logic_vector(3 downto 0);
begin
process(clock_enable, CLR)
begin
if CLR='1' then X <= "0000";
elsif (clock_enable'event and clock_enable='1') then X <= D;
end if;
end process;
Q <= X when CE = '1' else "XXXX";
end ARCH_REGISTRE;
```

 1. Fichier « Registre.vhd » :

Commentaire : Si CE=1, l'entrée de registre sera recopié dans la sortie ,si non la sortie est un état inconnu fort

- On tape les lignes de commande suivantes dans la fenêtre *transcript* :
force CE 1 0,0 350
force D 0000 0,0001 60,0010 120,0011 180,0100 240
force clr 0
run 500
pour clock_enable a une période de 100ns
- La simulation donne les résultats suivants :



```

LIBRARY ieee;
USE ieee.std_logic_1164.all;
entity REGISTRE_TB is
end REGISTRE_TB;
architecture TB4 of REGISTRE_TB is
component REGISTRE
port (clock_enable, CLR, CE :in std_logic;
      D :in std_logic_vector(3 downto 0);
      Q :out std_logic_vector(3 downto 0));
end component;
signal clock_enable, CLR, CE :std_logic;
signal D :std_logic_vector(3 downto 0);
signal Q :std_logic_vector(3 downto 0);
begin
R:REGISTRE port map (clock_enable, CLR, CE, D, Q);
process
begin
clock_enable <= '0';
wait for 5 ns;
clock_enable <= '1';
wait for 5 ns;
end process;
process
begin
CE <= '1';
wait for 120 ns;
CE <= '0';
wait for 20 ns;
end process;

```

2. Fichier « REGISTRE_TB » :

```


process
begin
CLR <= '0';
wait for 80 ns;
CLR <= '1';
wait for 40 ns;
end process;
process
variable C:integer :=0;
begin

```

```

    --case1
    wait for 5 ns;
    D <= "0000";
    wait for 15 ns;
    assert(Q = "0000") report "Error1!" severity Error;
    if (Q /= "0000")then
    C:=C+1;
end if;
--case2
wait for 5 ns;
    D <= "0011";
    wait for 15 ns;
    assert(Q = "0011") report "Error2!" severity Error;
    if (Q /= "0011")then
    C:=C+1;
end if;
--case3
    wait for 5 ns;
    D <= "0110";
    wait for 15 ns;
    assert(Q = "0110") report "Error3!" severity Error;
    if (Q /= "0110")then
    C:=C+1;
end if;
--case4
    wait for 5 ns;
    D <= "1001";
    wait for 15 ns;
    assert(Q = "1001") report "Error4!" severity Error;
    if (Q /= "1001")then
    C:=C+1;
end if;

```
 
```

--case5
    wait for 5 ns;
    D <= "1101";
    wait for 15 ns;
    assert (Q = "0000") report "Error5!" severity Error;
    if (Q /= "0000")then
        C:=C+1;
    end if;
--case6
    wait for 5 ns;
    D <= "1111";
    wait for 15 ns;
    assert (Q = "0000") report "Error6!" severity Error;
    if (Q /= "0000")then
        C:=C+1;
    end if;
--case7
    wait for 5 ns;
    D <= "0001";
    wait for 15 ns;
    assert (Q = "XXXX") report "Error5!" severity Error;
    if (Q /= "XXXX")then
        C:=C+1;
    end if;

    -- summary of testbench
    if (C=0) then
        assert false
        report "Testbench of REGISTRE_TB completed successfully!"
        severity note;
    else
        assert true
        report " Something wrong,try again"
        severity error;
    end if;
    wait;
end process;
end TB4;


```

- La simulation donne les résultats suivants :

III. Conception des multiplexeurs et démultiplexeurs :

1. Conception des multiplexeurs :

1.1 Multiplexeur 2 vers 1 :

 

Sc1	E_UAL
0	Res
1	A

a. Fichier « MUX1.vhd » :

On tape les lignes de commande suivantes dans la fenêtre *transcript* :

```
force A 0000 0,0001 30,0010 60  
force res 0110 0,1111 40,1010 80  
force Sc1 0 0,1 35  
run 80
```

La simulation donne les résultats suivants :

```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;  
entity MUX1 is  
port ( A,Res:in std_logic_vector(3 downto 0);  
       Sc1:in std_logic;  
       E_UAL:out std_logic_vector(3 downto 0));  
end MUX1;  
architecture arch_MUX1 of MUX1 is  
begin  
E_UAL <= A when Sc1 = '0' else  
         Res;  
end arch_MUX1;
```

b. Fichier « MUX1_TB.vhd » :



```

library ieee;
use ieee.std_logic_1164.all;

entity MUX1_TB is
end MUX1_TB;

architecture TB5 of MUX1_TB is
component MUX1
port ( A,Res:in std_logic_vector(3 downto 0);
       Sc1:in std_logic;
       E_UAL:out std_logic_vector(3 downto 0));
end component;
signal A,Res:std_logic_vector(3 downto 0);
signal Sc1:std_logic;
signal E_UAL:std_logic_vector(3 downto 0);
begin
    M1: MUX1 port map (A,Res,Sc1,E_UAL);
process
variable C:integer :=0;
begin
    -- case1
    A <= "1000";
    Res <= "0100";
    Sc1 <= '0';
    wait for 10ns;
    assert (E_UAL = "1000") report "Error!" Severity error;
    if(E_UAL /= "1000") then
        C:=C+1;
    end if;
end process;


```

```


-- case2
A <= "1000";
Res <= "0100";
Sc1 <= '1';
wait for 10ns;
assert (E_UAL = "0100") report "Error!" Severity error;
if(E_UAL /= "0100") then
C:=C+1;
end if;
-- summary of testbench
if (C=0) then
assert false
report "Testbench of MUX1 completed successfully!"
severity note;
else
assert true
report " Something wrong,try again"
severity error;
end if;
wait;
end process;
end TB5;

```

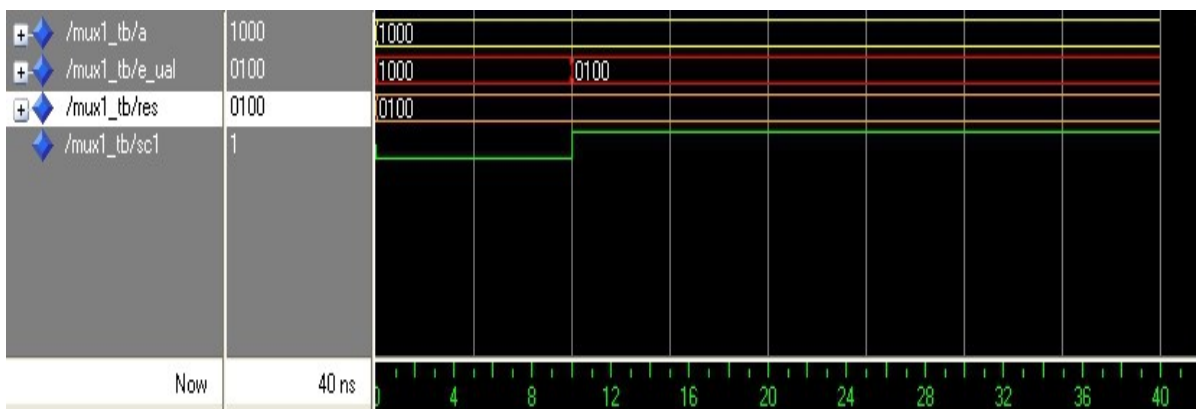La simulation donne les résultats suivants :



1.2 Multiplexeur 4 vers 1

 

Sc2	Res
00	S_R0
01	S_R1
10	S_R2
11	S_R3

a. Fichier « MUX2.vhd » :

Sc2e
s


```

LIBRARY ieee;
USE ieee.std_logic_1164.all;
entity MUX2 is
port ( S_R0,S_R1,S_R2,S_R3:in std_logic_vector(3 downto 0);
      Sc2:in std_logic_vector(1 downto 0);
      Res:out std_logic_vector(3 downto 0));
end MUX2;
architecture arch_MUX2 of MUX2 is
begin
  Res <= S_R0 when Sc2="00"else
         S_R1 when Sc2 ="01"else
         S_R2 when Sc2="10"else
         S_R3;
end arch_MUX2;

```

- On tape les lignes de commande suivantes dans la fenêtre *transcript* :
force S_R0 0000 0,0001 20
force S_R1 0010 0,0011 10
force S_R2 0100 0,0101 15
force S_R3 0111 0,1000 10
force Sc2 00 0,01 5,10 10,11 15
run 20

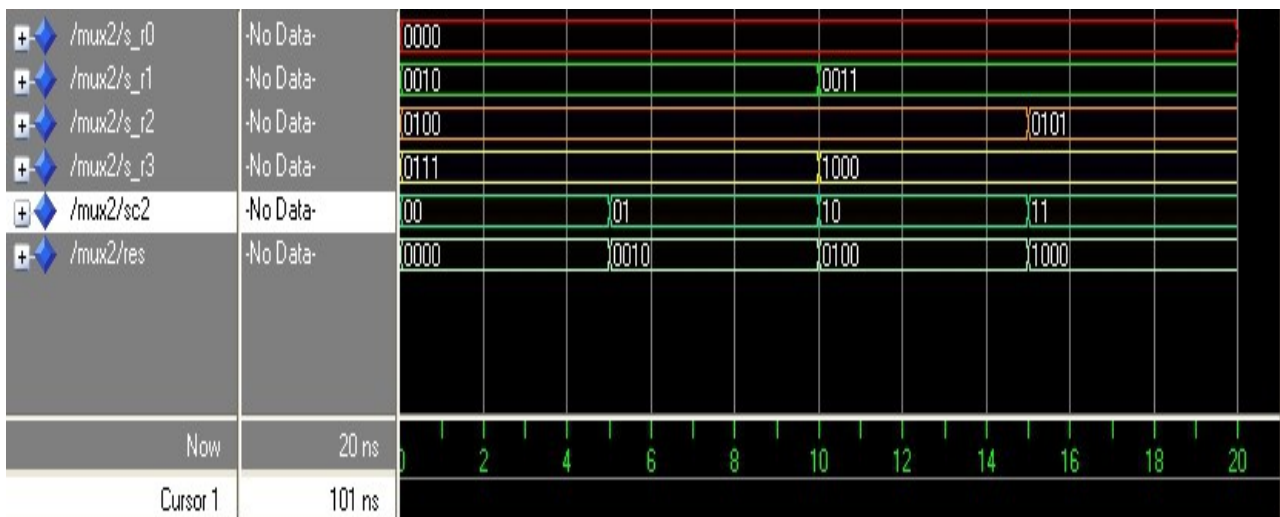- La simulation donne les résultats suivants :



b. Fichier « MUX2_TB » :

```
library ieee;
use ieee.std_logic_1164.all;

entity MUX2_TB is
end MUX2_TB;

architecture TB6 of MUX2_TB is
component MUX2
port ( S_R0,S_R1,S_R2,S_R3:in std_logic_vector(3 downto 0);
      Sc2:in std_logic_vector(1 downto 0);
      Res:out std_logic_vector(3 downto 0));
end component;
Signal S_R0,S_R1,S_R2,S_R3:std_logic_vector(3 downto 0);
Signal Sc2:std_logic_vector(1 downto 0);
Signal Res:std_logic_vector(3 downto 0);
begin
    M2: MUX2 port map (S_R0,S_R1,S_R2,S_R3,Sc2,Res);
process
variable C:integer :=0;
begin
    -- case1
    S_R0 <= "1000";
    S_R1 <= "0100";
    S_R2 <= "0001";
    S_R3 <= "1001";
    Sc2 <= "00";
    wait for 10ns;
    assert (Res = "1000") report "Error!" Severity error;
    if(Res /= "1000") then
        C:=C+1;
    end if;

    -- case2
    S_R0 <= "1000";
    S_R1 <= "0100";
    S_R2 <= "0001";
    S_R3 <= "1001";
    Sc2 <= "01";
    wait for 10ns;
    assert (Res = "0100") report "Error!" Severity error;
    if(Res /= "0100") then
        C:=C+1;
    end if;
    -- case3
    S_R0 <= "1000";
    S_R1 <= "0100";
    S_R2 <= "0001";
    S_R3 <= "1001";
    Sc2 <= "10";
    wait for 10ns;
    assert (Res = "0001") report "Error!" Severity error;
    if(Res /= "0001") then
        C:=C+1;
    end if;
end process;
end if;
```

```


--case4
  S_R0 <= "1000";
  S_R1 <= "0100";
  S_R2 <= "0001";
  S_R3 <= "1001";
  sc2 <= "11";
  wait for 10ns;
  assert (Res = "1001") report "Error!" Severity error;
  if(Res /= "1001") then
    C:=C+1;
  end if;
-- summary of testbench
if (C=0) then
  assert false
  report "Testbench of MUX2 completed successfully!"
  severity note;
else
  assert true
  report " Something wrong,try again"
  severity error;
end if;
wait;
end process;
end TB6;

```

La simulation donne les résultats suivants :

Signal	Value	0	4	8	12	16	20	24	28	32	36	40
/mux2_tb/res	-No Data-	1000		0100			0001			1001		
/mux2_tb/s_r0	-No Data-	1000										
/mux2_tb/s_r1	-No Data-	0100										
/mux2_tb/s_r2	-No Data-	0001										
/mux2_tb/s_r3	-No Data-	1001										
/mux2_tb/sc2	-No Data-	00		01			10			11		
Now	40 ns	0 4 8 12 16 20 24 28 32 36 40										
Cursor 1	647 ns											

2. Conception de démultiplexeur :

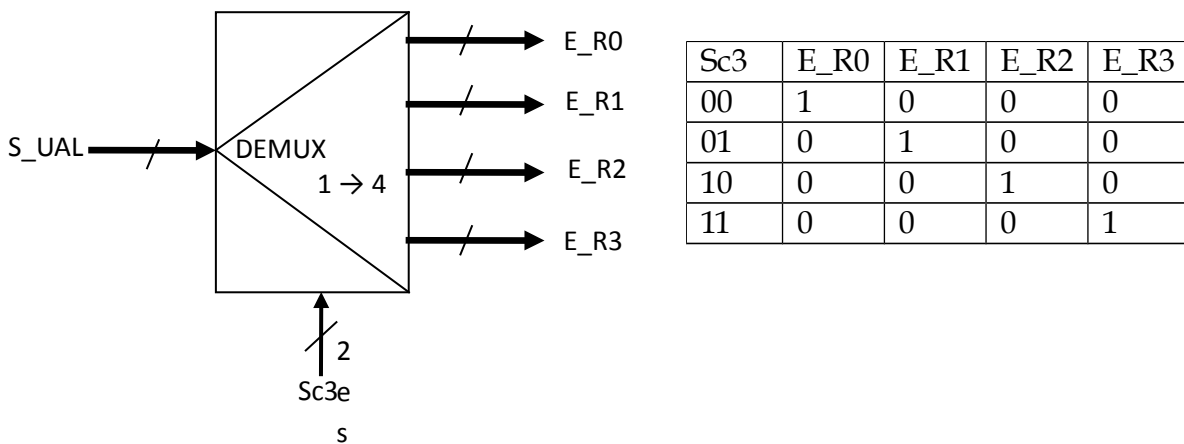

a. Fichier « DEMUX.vhd » :

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;
entity DEMUX is
port ( S_UAL:in std_logic_vector(3 downto 0);
      Sc3:in std_logic_vector(1 downto 0);
      E_R0,E_R1,E_R2,E_R3:out std_logic_vector(3 downto 0));
end DEMUX;
architecture arch_DEMUX of DEMUX is
begin
  E_R0 <= S_UAL when Sc3 = "00" else
    "XXXX";
  E_R1 <= S_UAL when Sc3 = "01" else
    "XXXX";
  E_R2 <= S_UAL when Sc3 = "10" else
    "XXXX";
  E_R3 <= S_UAL when Sc3 = "11" else
    "XXXX";
end arch_DEMUX;

```


- On tape les lignes de commande suivantes dans le transcript :

force S_UAL 0000 0,0001 10,0011 20,0100 40

force Sc3 00 0,01 10,10 20,11 40

run 50

 - La simulation donne les résultats suivants :



b. Fichier « DEMUX_TB » :

```
library ieee;
use ieee.std_logic_1164.all;

entity DEMUX_TB is
end DEMUX_TB;

architecture TB7 of DEMUX_TB is
component DEMUX
port ( S_UAL:in std_logic_vector(3 downto 0);
      Sc3:in std_logic_vector(1 downto 0);
      E_R0,E_R1,E_R2,E_R3:out std_logic_vector(3 downto 0));
end component;
Signal S_UAL:std_logic_vector(3 downto 0);
Signal Sc3:std_logic_vector(1 downto 0);
Signal E_R0,E_R1,E_R2,E_R3:std_logic_vector(3 downto 0);
begin
  DM: DEMUX port map (S_UAL,Sc3,E_R0,E_R1,E_R2,E_R3);
process
variable C:integer :=0;
begin

  -- case1
  S_UAL <= "1000";
  Sc3 <= "00";
  wait for 10ns;
  assert (E_R0 = "1000") report "Error!" Severity error;
  assert (E_R1 = "XXXX") report "Error!" Severity error;
  assert (E_R2 = "XXXX") report "Error!" Severity error;
  assert (E_R3 = "XXXX") report "Error!" Severity error;
  if(E_R0 /= "1000" or E_R1 /= "XXXX" or E_R2 /= "XXXX" or E_R3 /= "XXXX") then
    C:=C+1;
  end if;

  -- case2
  S_UAL <= "1000";
  Sc3 <= "01";
  wait for 10ns;
  assert (E_R0 = "XXXX") report "Error!" Severity error;
  assert (E_R1 = "1000") report "Error!" Severity error;
  assert (E_R2 = "XXXX") report "Error!" Severity error;
  assert (E_R3 = "XXXX") report "Error!" Severity error;
  if(E_R0 /= "XXXX" or E_R1 /= "1000" or E_R2 /= "XXXX" or E_R3 /= "XXXX") then
    C:=C+1;
  end if;

  -- case3
  S_UAL <= "1000";
  Sc3 <= "10";
  wait for 10ns;
  assert (E_R0 = "XXXX") report "Error!" Severity error;
  assert (E_R1 = "XXXX") report "Error!" Severity error;
  assert (E_R2 = "1000") report "Error!" Severity error;
  assert (E_R3 = "XXXX") report "Error!" Severity error;
  if(E_R0 /= "XXXX" or E_R1 /= "XXXX" or E_R2 /= "1000" or E_R3 /= "XXXX") then
    C:=C+1;
  end if;


  -- case4
  S_UAL <= "1000";
  Sc3 <= "11";
  wait for 10ns;
  assert (E_R0 = "XXXX") report "Error!" Severity error;
  assert (E_R1 = "XXXX") report "Error!" Severity error;
  assert (E_R2 = "XXXX") report "Error!" Severity error;
  assert (E_R3 = "1000") report "Error!" Severity error;
  if(E_R0 /= "XXXX" or E_R1 /= "XXXX" or E_R2 /= "XXXX" or E_R3 /= "1000") then
    C:=C+1;
  end if;
end process;
end TB7;
```

```


-- summary of testbench
if (C=0) then
  assert false
  report "Testbench of DEMUX completed successfully!"
  severity note;
else
  assert true
  report " Something wrong,try again"
  severity error;
end if;
wait;
end process;
end TB7;

```

 La simulation donne les résultats suivants :



IV. Conception du contrôleur :

 

- Le bit 3 de l'instruction permet de préciser si l'on souhaite effectuer une opération sur les entrées A et B ou sur B et une donnée provenant de l'un des registres => C'est le signal de sélection de multiplexeur 2 vers 1.
- Les bits 5 et 4 permettent de sélectionner le registre dans lequel une donnée servira à effectuer un calcul avec l'opérande B => C'est le signal de sélection de multiplexeur 4 vers 1.
- Les bits 7 et 6 permettent de sélectionner le registre dans le quel le résultat de l'UAL sera stocké => C'est le signal de sélection du démultiplexeur 1 vers 4.

Fichier « CONTROL1.vhd » :



```

LIBRARY ieee;
USE ieee.std_logic_1164.all;
entity controll1 is
port( Instr:in std_logic_vector(7 downto 0);
      Sc1:out std_logic;
      Sc2,Sc3:out std_logic_vector(1 downto 0);
      Code_OP:out std_logic_vector(2 downto 0);
      CE0,CE1,CE2,CE3:out std_logic);
end controll1;
architecture arch_controll1 of controll1 is
    signal S:std_logic_vector(1 downto 0);
begin
    Code_OP <= Instr(2) & Instr(1) & Instr(0);
    Sc1 <= Instr(3);
    Sc2 <= Instr(5) & Instr(4);
    Sc3 <= Instr(7) & Instr(6);
    S <= Instr(7) & Instr(6);
    CE0 <= '1' when S="00" else
           '0';
    CE1 <= '1' when S="01" else
           '0';
    CE2 <= '1' when S="10" else
           '0';
    CE3 <= '1' when S="11" else
           '0';
end arch_controll1;

```

- On tape les lignes de commande dans le transcript :
force Instr 01011111 0,01010000 10,11111010 20,10101010 30,01100110
40,11111111 50,00000000 60
run 70
- La simulation donne les résultats suivants :

 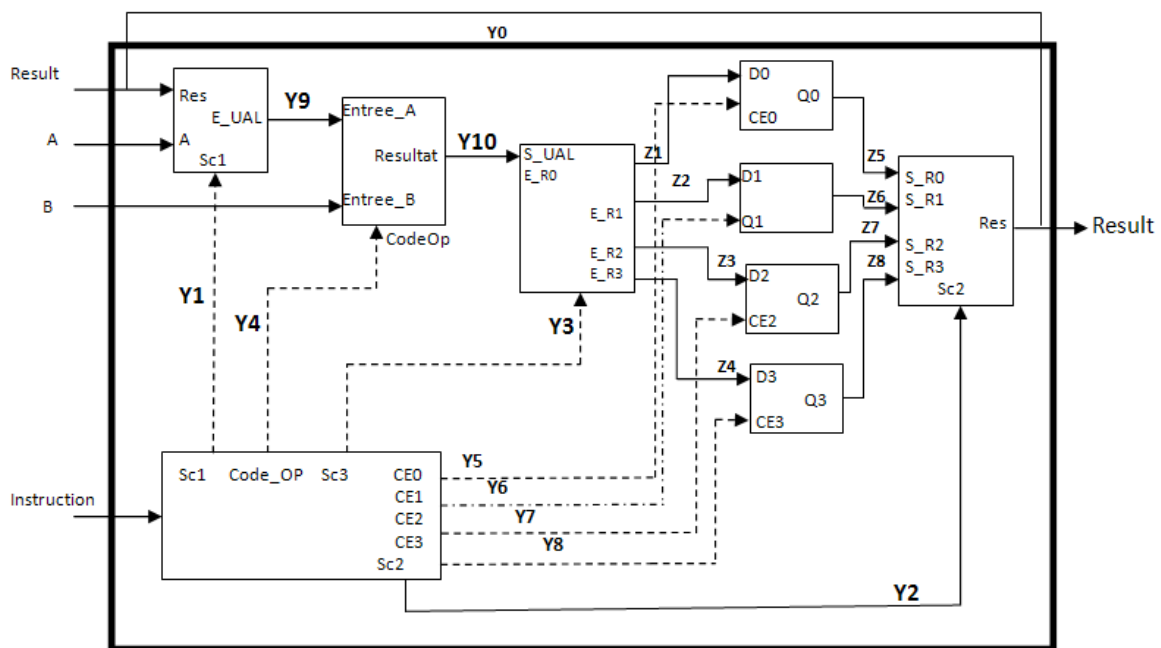V. Conception final du mini-calculateur :



- Fichier « mini_calcul.vhd » :

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
entity MINI_CALCUL is
port ( A,B:in std_logic_vector(3 downto 0);
      Instruction:in std_logic_vector(7 downto 0);
      Clock,CLR:in std_logic;
      Result:inout std_logic_vector(3 downto 0);
      A_SUP_B,A_INF_B,A_EGAL_B,NEG,ZERO,OVFL:out std_logic);
end MINI_CALCUL;
architecture arch_mini_calcul of MINI_CALCUL is
-- Multiplexeur 2 vers 1
component MUX1
port( A,Res:in std_logic_vector(3 downto 0);
      Scl:in std_logic;
      E_UAL:out std_logic_vector(3 downto 0));
end component;
-- UAL
component Unite
port ( entree_A,entree_B: in std_logic_vector(3 downto 0);
      CodeOP:in std_logic_vector(2 downto 0);
      resultat:out std_logic_vector(3 downto 0);
      S_A_SUP_B,S_A_INF_B,S_A_EGAL_B,S_NEG,S_ZERO,S_OVFL:out std_logic);
end component;
-- Demultiplexeur
component DEMUX
port ( S_UAL:in std_logic_vector(3 downto 0);
      Sc3:in std_logic_vector(1 downto 0);
      E_R0,E_R1,E_R2,E_R3:out std_logic_vector(3 downto 0));
end component;
```

```

--Registre
component REGISTRE
port (clock_enable,CLR,CE :in std_logic;
      D :in std_logic_vector(3 downto 0);
      Q :out std_logic_vector(3 downto 0));
end component;
-- Multiplexeur 4 vers 1
component MUX2
port ( S_R0,S_R1,S_R2,S_R3:in std_logic_vector(3 downto 0);
      Sc2:in std_logic_vector(1 downto 0);
      Res:out std_logic_vector(3 downto 0));
end component;
--Controleur
component controll1
port( Instr:in std_logic_vector(7 downto 0);
      Sc1:out std_logic;
      Sc2,Sc3:out std_logic_vector(1 downto 0);
      Code_OP:out std_logic_vector(2 downto 0);
      CE0,CE1,CE2,CE3:out std_logic);
end component;
Signal Y1,Y5,Y6,Y7,Y8:std_logic;
Signal Y2,Y3:Std_logic_vector(1 downto 0);
Signal Y4:Std_logic_vector(2 downto 0);
Signal Y0,Y9,Y10,Z1,Z2,Z3,Z4,Z5,Z6,Z7,Z8:Std_logic_vector(3 downto 0);


begin
  C1:controll1 port map (Instruction,Y1,Y2,Y3,Y4,Y5,Y6,Y7,Y8);
  C2:MUX1 port map(A,Result,Y1,Y9);
  C3:Unite port map (Y9,B,Y4,Y10,A_SUP_B,A_INF_B,A_EGAL_B,NEG,ZERO,OVFL);
  C4:DEMUX port map (Y10,Y3,Z1,Z2,Z3,Z4);
  C5:REGISTRE port map(Clock,CLR,Y5,Z1,Z5);
  C6:REGISTRE port map(Clock,CLR,Y6,Z2,Z6);
  C7:REGISTRE port map(Clock,CLR,Y7,Z3,Z7);
  C8:REGISTRE port map(Clock,CLR,Y8,Z4,Z8);
  C9:MUX2 port map (Z5,Z6,Z7,Z8,Y2,Y0);
  Result <= Y0 ;
end arch_mini_calcul;

```

Exercices en VHDL

I. Modélisation d'un décodeur 7

segments :

 

1. Table de vérité :

E1	E2	E3	E4	SEG_A	SEG_B	SEG_C	SEG_D	SEG_E	SEG_F	SEG_G
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1

2. Fichier « dec7seg.vhd »

```


LIBRARY ieee;
USE ieee.std_logic_1164.all;
entity dec7seg is
port( BCD: in std_logic_vector (3 downto 0);
      SEGS: out std_logic_vector(6 downto 0));
end dec7seg;
architecture bhv of dec7seg is
begin
  with BCD select
    SEGS <= "1111110" when "0000",
           "0110000" when "0001",
           "1101101" when "0010",
           "1111001" when "0011",
           "0110011" when "0100",
           "1011011" when "0101",
           "1011111" when "0110",
           "1110000" when "0111",
           "1111111" when "1000",
           "1111011" when "1001",
           "-----" when others;
end bhv;

```


On tape les lignes de commande suivantes dans la fenêtre *transcript* :

- force bcd 0000 0,0001 20,0010 40,0011 60,0100 80,0101 100,0110 120,0111
140,1000 160,1001 180,1010 200,1011 220
- run 240

 La simulation donne les résultats suivants :



3. Fichier « dec7seg_TB.vhd »

```

library ieee;
use ieee.std_logic_1164.all;

entity dec7seg_TB is
end dec7seg_TB;

architecture TB2 of dec7seg_TB is
component dec7seg
port( BCD: in std_logic_vector (3 downto 0);
      SEGS: out std_logic_vector(6 downto 0));
end component;
signal BCD:std_logic_vector (3 downto 0);
signal SEGS:std_logic_vector(6 downto 0);
begin
  dec:dec7seg port map (BCD,SEGS);
  process
    variable C:integer:=0;
    begin
      --case 1
      BCD <= "0000";
      wait for 2 ns;
      assert(SEGS = "1111110")
      report "SEGS error!" severity error;
      if ( SEGS /= "1111110") then
        C:= C +1;
      end if;
      --case 2
      BCD <= "0001";
      wait for 2 ns;
      assert(SEGS = "0110000")
      report "SEGS error!" severity error;
      if ( SEGS /= "0110000") then
        C:= C +1;
      end if;
    end process;
  
```

```

--case 3
BCD <= "0010";
wait for 2 ns;
assert(SEGS = "1101101")
report "SEGS error!" severity error;
if ( SEGS /= "1101101") then
  C:= C +1;
end if;
--case 4
BCD <= "0011";
wait for 2 ns;
assert(SEGS = "1111001")
report "SEGS error!" severity error;
if ( SEGS /= "1111001") then
  C:= C +1;
end if;
--case 5
BCD <= "0100";
wait for 2 ns;
assert(SEGS = "0110011")
report "SEGS error!" severity error;
  if ( SEGS /= "0110011") then
    C:= C +1;
  end if;
--case 6
BCD <= "0101";
wait for 2 ns;
assert(SEGS = "1011011")
report "SEGS error!" severity error;
if ( SEGS /= "1011011") then
  C:= C +1;
end if;
--case 7
BCD <= "0110";
wait for 2 ns;
assert(SEGS = "1011111")
report "SEGS error!" severity error;
  if ( SEGS /= "1011111") then
    C:= C +1;
  end if;
--case 8
BCD <= "0111";
wait for 2 ns;
assert(SEGS = "1110000")
report "SEGS error!" severity error;
  if ( SEGS /= "1110000") then
    C:= C +1;
  end if;
--case 9
BCD <= "1000";
wait for 2 ns;
assert(SEGS = "1111111")
report "SEGS error!" severity error;
  if ( SEGS /= "1111111") then

```

```

C:= C +1;
end if;
--case 10
BCD <= "1001";
wait for 2 ns;
assert(SEGS = "1111011")
report "SEGS error!" severity error;
  if ( SEGS /= "1111011") then
    C:= C +1;
  end if;
-- lorsque l'entree BCD dépasse 9
--case 11
BCD <= "1010";
wait for 2 ns;
assert(SEGS = "-----")
report "SEGS error!" severity error;
  if ( SEGS /= "-----") then
    C:= C +1;
  end if;
--case 12
BCD <= "1011";
wait for 2 ns;
assert(SEGS = "-----")
report "SEGS error!" severity error;
  if ( SEGS /= "-----") then
    C:= C +1;
  end if;
--case 13
BCD <= "1100";
wait for 2 ns;
assert(SEGS = "-----")
report "SEGS error!" severity error;
  if ( SEGS /= "-----") then
    C:= C +1;
  end if;
--case 14
BCD <= "1101";
wait for 2 ns;
assert(SEGS = "-----")
report "SEGS error!" severity error;
  if ( SEGS /= "-----") then
    C:= C +1;
  end if;
--case 15
BCD <= "1110";
wait for 2 ns;
assert(SEGS = "-----")
report "SEGS error!" severity error;
  if ( SEGS /= "-----") then
    C:= C +1;
  end if;
--case 16
BCD <= "1111";
wait for 2 ns;
assert(SEGS = "-----")
report "SEGS error!" severity error;


```

```


        if ( SEGS /= "-----") then
            C:= C +1;
        end if;
-- summury of test bench
if (C=0) then
assert false
report "Testbench of compara_4b completed successfully!"
severity note;
else
assert true
report " Something wrong,try again"
severity error;
end if;
wait;
end process;
end TB2;

```

 La simulation du test bench du décodeur 7 segments donne les résultats suivants :



 II. Modélisation d'un compteur synchrone :



1. Fichier « compteur.vhd » :

```
library ieee ;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;


entity counter is

generic(n: natural := 3);
port( clk: in std_logic;
      rst: in std_logic;
      count: out integer range 0 to n-1);
end counter;

architecture behv of counter is


begin
    process(clk, rst)
        variable X :integer range 0 to n-1;
    begin
        if (rst='1')then X:=0;
        elsif(clk='1' and clk'event) then
            if X > n-1 then X := 0;
            else X := X + 1;
            end if;
            end if;
            count <= X;
        end process;
    end behv;
```

 - On tape les lignes de commande dans le transcript :
Force clk 1 0, 0 {50 ns} -r 100
Force rst 0 0
- La simulation donne les résultats suivants :



On change la valeur du N, et on lui donne cette fois la valeur 12 ,(*generic(n: natural := 12);*)

 Le résultat de la simulation est le suivant :



2. Fichier « compteur_TB.vhd » :

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;

entity counter_TB is
end counter_TB;

architecture TB8 of counter_TB is

    component counter
        port (clk: in std_logic;
              rst: in std_logic;
              count: out integer range 0 to 1);
    end component;

    Signal clk:std_logic;
    Signal rst:std_logic;
    Signal count: integer range 0 to 1;
begin

```

```

U_counter: counter port map (clk,rst,count);
process
begin
clk <= '0';
  wait for 5 ns;
clk <= '1';
  wait for 5 ns;
end process;


process

variable C: integer :=0;


begin
rst <= '1';
wait for 5 ns;
rst <= '0';
-- test case 1
wait for 5 ns;
assert (count =1) report "Error1" severity error;
if (count/=1) then
  C:= C+1;
end if;
-- test case 2
wait for 10 ns;
assert (count = 2) report "Error2" severity error;
if (count/=2) then
  C:= C+1;
end if;
-- summary of testbench
  if (C=0) then
    assert false
    report "Testbench of counter completed successfully!"
    severity note;
  else
    assert true
    report " Something wrong,try again"
    severity error;
  end if;
  wait;
end process;
end TB8;

```

 
Remarque : le testbench est fait pour N = 3




⇒ Simulation :

 

IV. Modélisation d'une bascule JK:

 

1. Fichier « JK.vhd » :

 

```

end process;

Q <= state;
Qbar <= not state;

end behv;

```

- On tape les lignes de commande suivante dans le transcript :

Force clk 1 0, 0 {50 ns} -r 100

force reset 1 0,0 20

force j 0 0,1 110

force k 0 0,1 40,0 110,1 210

run 300

- La simulation donne les résultats suivants :

2. Fichier « JK_TB.vhd » :

```

library ieee;
use ieee.std_logic_1164.all;

entity jk_TB is
end jk_TB;

architecture TB10 of jk_TB is

    signal J, K: std_logic;
    signal clk: std_logic;
    signal reset: std_logic;
    signal Q, Qbar: std_logic;

    component JK_FF is
    port ( clk: in std_logic;
          J, K: in std_logic;
          reset: in std_logic;
          Q, Qbar: out std_logic);
    end component;

begin

    C: JK_FF port map (clk, J, K, reset, Q, Qbar);
    process
    begin
    clk <= '0';
    wait for 5 ns;
    clk <= '1';
    wait for 5 ns;
    end process;

```

```

    process
    variable cnt: integer := 0;
    begin

        reset <= '1';
        wait for 25 ns;

        reset <= '0';
        wait for 10 ns;

        -- case 1
        J <= '0';
        K <= '1';
        wait for 15 ns;
        assert (Q='0') report "Error1!" severity error;
        if (Q/='0') then
            cnt := cnt + 1;
        end if;

        -- case 2
        wait for 5 ns;
        J <= '1';
        K <= '0';
        wait for 15 ns;
        assert (Q='1') report "Error2!" severity error;
        if (Q/='0') then
            cnt := cnt + 1;
        end if;

        wait for 15 ns;
        assert (Q='1') report "Error2!" severity error;
        if (Q/='0') then
            cnt := cnt + 1;
        end if;

        -- case 3
        wait for 5 ns;
        J <= '1';
        K <= '1';
        wait for 15 ns;
        assert (Q='0') report "Error3!" severity error;
        if (Q/='0') then
            cnt := cnt + 1;
        end if;

        -- summary of all the tests
        if (cnt=0) then
            assert false
            report "Testbench of Bascule JK completed successfully!"
            severity note;
        else
            assert true
            report "Something wrong, try again"
            severity error;
        end if;

        wait;

    end process;

end TB10;

```

⇒ Simulation :

